

**CURRENT ELECTRICITY**

1. A wire of length 10 cm and radius  $\sqrt{7} \cdot 10^{-4}$  m connected across the right gap of a meter bridge. When a resistance of  $4.5 \Omega$  is connected on the left gap by using a resistance box, the balance length is found to be at 60 cm from the left end. If the resistivity of the wire is  $R \times 10^{-7} \Omega\text{m}$ , then value of R is :

- (1) 63 (2) 70  
 (3) 66 (4) 35

2. A wire of resistance R and length L is cut into 5 equal parts. If these parts are joined parallelly, then resultant resistance will be :

- (1)  $\frac{1}{25}R$  (2)  $\frac{1}{5}R$   
 (3) 25 R (4) 5 R


3. Wheatstone bridge principle is used to measure the specific resistance ( $S_1$ ) of given wire, having length L, radius r. If X is the resistance of wire, then specific resistance is :  $S_1 = X \left( \frac{\pi r^2}{L} \right)$ . If the length of the wire gets doubled then the value of specific resistance will be :

- (1)  $\frac{S_1}{4}$  (2)  $2S_1$   
 (3)  $\frac{S_1}{2}$  (4)  $S_1$

4. A current of  $200 \text{ mA}$  deflects the coil of a moving coil galvanometer through  $60^\circ$ . The current to cause deflection through  $\frac{\pi}{10}$  radian is :

- (1)  $30 \text{ mA}$   
 (2)  $120 \text{ mA}$   
 (3)  $60 \text{ mA}$   
 (4)  $180 \text{ mA}$

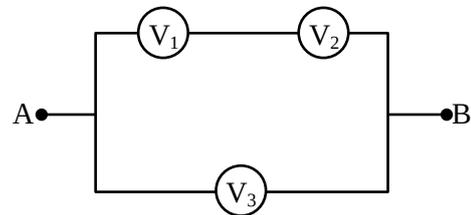5. Three voltmeters, all having different internal resistances are joined as shown in figure. When some potential difference is applied across A and B, their readings are  $V_1$ ,  $V_2$  and  $V_3$ . Choose the correct option.



- (1)  $V_1 = V_2$  (2)  $V_1 \neq V_3 - V_2$   
 (3)  $V_1 + V_2 > V_3$  (4)  $V_1 + V_2 = V_3$

6. The electric current through a wire varies with time as  $I = I_0 + \beta t$ , where  $I_0 = 20 \text{ A}$  and  $\beta = 3 \text{ A/s}$ . The amount of electric charge crossed through a section of the wire in 20 s is :

- (1) 80 C (2) 1000 C  
 (3) 800 C (4) 1600 C

7. A galvanometer having coil resistance  $10 \Omega$  shows a full scale deflection for a current of  $3 \text{ mA}$ . For it to measure a current of  $8 \text{ A}$ , the value of the shunt should be:


- (1)  $3 \times 10^{-3} \Omega$   
 (2)  $4.85 \times 10^{-3} \Omega$   
 (3)  $3.75 \times 10^{-3} \Omega$   
 (4)  $2.75 \times 10^{-3} \Omega$

8. The deflection in moving coil galvanometer falls from 25 divisions to 5 division when a shunt of  $24 \Omega$  is applied. The resistance of galvanometer coil will be :


- (1)  $12 \Omega$   
 (2)  $96 \Omega$   
 (3)  $48 \Omega$   
 (4)  $100 \Omega$

## CURRENT ELECTRICITY

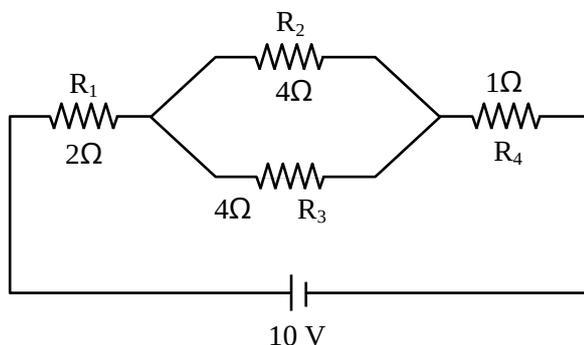
9. In the given circuit, the current in resistance  $R_3$  is :



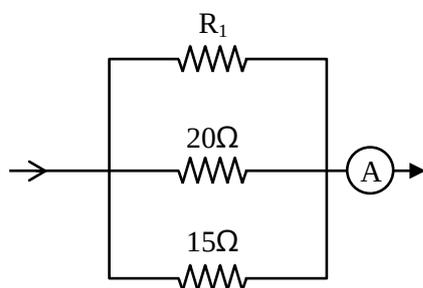- (1) 1 A  
 (2) 1.5 A  
 (3) 2 A  
 (4) 2.5 A
10. In the given circuit, the current flowing through the resistance  $20\Omega$  is 0.3 A, while the ammeter reads 0.9 A. The value of  $R_1$  is \_\_\_\_\_  $\Omega$ .



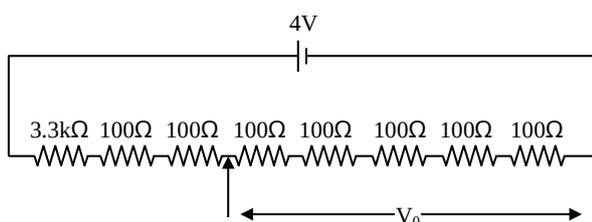11. A potential divider circuit is shown in figure. The output voltage  $V_0$  is




- (1) 4V  
 (2) 2 mV  
 (3) 0.5 V  
 (4) 12 mV

12. An electric toaster has resistance of  $60\Omega$  at room temperature ( $27^\circ\text{C}$ ). The toaster is connected to a 220 V supply. If the current flowing through it reaches 2.75 A, the temperature attained by toaster is around :
- (if  $\alpha = 2 \cdot 10^{-4} / ^\circ\text{C}$ )

- (1)  $694^\circ\text{C}$   
 (2)  $1235^\circ\text{C}$   
 (3)  $1694^\circ\text{C}$   
 (4)  $1667^\circ\text{C}$

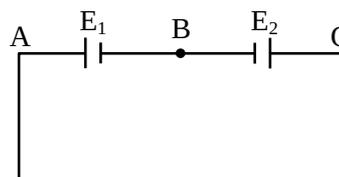13. Two cells are connected in opposition as shown. Cell  $E_1$  is of 8 V emf and  $2\Omega$  internal resistance; the cell  $E_2$  is of 2 V emf and  $4\Omega$  internal resistance. The terminal potential difference of cell  $E_2$  is:



14. When a potential difference  $V$  is applied across a wire of resistance  $R$ , it dissipates energy at a rate  $W$ . If the wire is cut into two halves and these halves are connected mutually parallel across the same supply, the energy dissipation rate will become:

- (1)  $1/4W$                       (2)  $1/2W$   
 (3)  $2W$                           (4)  $4W$

15. Two resistance of  $100\Omega$  and  $200\Omega$  are connected in series with a battery of 4 V and negligible internal resistance. A voltmeter is used to measure voltage across  $100\Omega$  resistance, which gives reading as 1 V. The resistance of voltmeter must be \_\_\_\_\_  $\Omega$ .




**CURRENT ELECTRICITY**

24. In an ammeter, 5% of the main current passes through the galvanometer. If resistance of the galvanometer is  $G$ , the resistance of ammeter will be :

- (1)  $\frac{G}{200}$                       (2)  $\frac{G}{199}$   
 (3)  $199 G$                       (4)  $200 G$

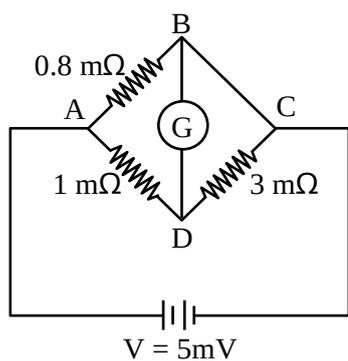25. To measure the temperature coefficient of resistivity  $\alpha$  of a semiconductor, an electrical arrangement shown in the figure is prepared. The arm BC is made up of the semiconductor. The experiment is being conducted at  $25^\circ\text{C}$  and resistance of the semiconductor arm is  $3 \Omega$ . Arm BC is cooled at a constant rate of  $2^\circ\text{C/s}$ . If the galvanometer  $G$  shows no deflection after 10s, then  $\alpha$  is :



- (1)  $-2 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$   
 (2)  $-1.5 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$   
 (3)  $-1 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$   
 (4)  $-2.5 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$

26. In a metre-bridge when a resistance in the left gap is  $2 \Omega$  and unknown resistance in the right gap, the balance length is found to be 40 cm. On shunting the unknown resistance with  $2 \Omega$ , the balance length changes by :

- (1) 22.5 cm  
 (2) 20 cm  
 (3) 62.5 cm  
 (4) 65 cm


27. The resistances of the platinum wire of a platinum resistance thermometer at the ice point and steam point are  $8 \Omega$  and  $10 \Omega$  respectively. After inserting in a hot bath of temperature  $400^\circ\text{C}$ , the resistance of platinum wire is :

- (1)  $2 \Omega$                       (2)  $16 \Omega$   
 (3)  $8 \Omega$                       (4)  $10 \Omega$

28. To measure the internal resistance of a battery, potentiometer is used. For  $R = 10 \Omega$ , the balance point is observed at  $\ell = 500 \text{ cm}$  and for  $R = 1 \Omega$  the balance point is observed at  $\ell = 400 \text{ cm}$ . The

internal resistance of the battery is approximately:  
 (1)  $0.2 \Omega$                       (2)  $0.4 \Omega$   
 (3)  $0.1 \Omega$                       (4)  $0.3 \Omega$

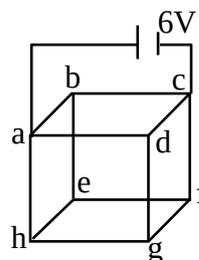29. Twelve wires each having resistance  $2 \Omega$  are joined to form a cube. A battery of 6 V emf is joined across point a and c. The voltage difference between e and f is \_\_\_\_\_ V.




30. An electric bulb rated  $50 \text{ W} - 200 \text{ V}$  is connected across a  $100 \text{ V}$  supply. The power dissipation of the bulb is :


- (1) 12.5 W                      (2) 25 W  
 (3) 50 W                      (4) 100 W

31. Two wires A and B are made up of the same material and have the same mass. Wire A has radius of 2.0 mm and wire B has radius of 4.0 mm. The resistance of wire B is  $2 \Omega$ . The resistance of wire A is \_\_\_\_\_  $\Omega$ .

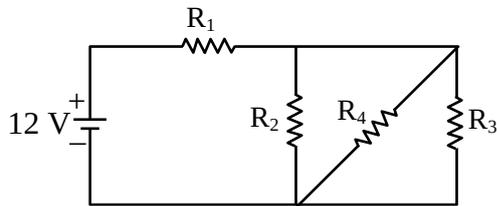
32. In the given figure  $R_1 = 10\Omega$ ,  $R_2 = 8\Omega$ ,  $R_3 = 4\Omega$  and  $R_4 = 8\Omega$ . Battery is ideal with emf 12V. Equivalent resistance of the circuit and current supplied by battery are respectively.



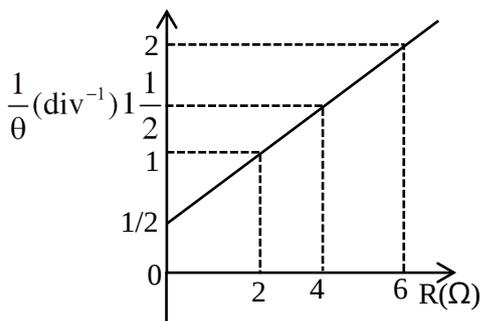- (1)  $12\Omega$  and 11.4 A  
 (2)  $10.5\Omega$  and 1.14 A  
 (3)  $10.5\Omega$  and 1 A  
 (4)  $12\Omega$  and 1 A
33. In the experiment to determine the galvanometer resistance by half-deflection method, the plot of  $\frac{1}{\theta}$  vs the resistance (R) of the resistance box is shown in the figure. The figure of merit of the galvanometer is .....  $\times 10^{-1}$  A/division. [The source has emf 2V].




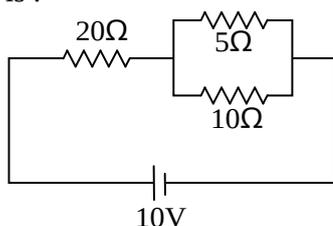34. A galvanometer of resistance  $100\Omega$  when connected in series with  $400\Omega$  measures a voltage of upto 10 V. The value of resistance required to convert the galvanometer into ammeter to read upto 10 A is  $x \times 10^{-2}\Omega$ . The value of x is :
- (1) 2 (2) 800  
 (3) 20 (4) 200
35. The ratio of heat dissipated per second through the resistance  $5\Omega$  and  $10\Omega$  in the circuit given below is :




- (1) 1 : 2 (2) 2 : 1  
 (3) 4 : 1 (4) 1 : 1

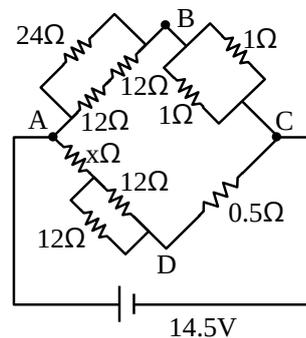36. A wire of resistance  $20\Omega$  is divided into 10 equal parts. A combination of two parts are connected in parallel and so on. Now resulting pairs of parallel combination are connected in series. The equivalent resistance of final combination is \_\_\_\_\_  $\Omega$ .
37. The value of unknown resistance (x) for which the potential difference between B and D will be zero in the arrangement shown, is :



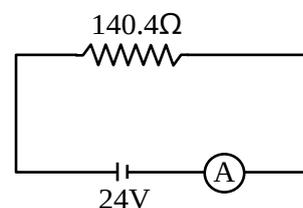- (1)  $3\Omega$  (2)  $9\Omega$   
 (3)  $6\Omega$  (4)  $42\Omega$
38. A wire of resistance R and radius r is stretched till its radius became  $r/2$ . If new resistance of the stretched wire is x R, then value of x is \_\_\_\_\_.
39. The number of electrons flowing per second in the filament of a 110 W bulb operating at 220 V is : (Given  $e = 1.6 \times 10^{-19}$  C)
- (1)  $31.25 \times 10^{17}$  (2)  $6.25 \times 10^{18}$   
 (3)  $6.25 \times 10^{17}$  (4)  $1.25 \times 10^{19}$
40. In the given figure an ammeter A consists of a  $240\Omega$  coil connected in parallel to a  $10\Omega$  shunt. The reading of the ammeter is \_\_\_\_\_ mA.





**SOLUTIONS**
**1. Ans. (3)**
**Sol.** For null point,

$$\frac{4.5}{60} = \frac{R}{40}$$

$$\text{Also, } R = \frac{\rho l}{A} = \frac{\rho l}{\pi r^2}$$

$$4.5 \cdot 40 = \rho \cdot \frac{0.1}{\pi \cdot 7 \cdot 10^{-8}} \cdot 60$$

$$\rho = 66 \cdot 10^{-7} \Omega \cdot \text{m}$$

**2. Ans. (1)**
**Sol.** Resistance of each part =  $\frac{R}{5}$ 

$$\text{Total resistance} = \frac{1}{5} \cdot \frac{R}{5} = \frac{R}{25}$$

**3. Ans. (4)**
**Sol.** As specific resistance does not depend on dimension of wire so, it will not change.

**4. Ans. (3)**
**Sol.**  $i \propto \theta$  (angle of deflection)

$$\therefore \frac{i_2}{i_1} = \frac{\theta_2}{\theta_1} \Rightarrow \frac{i_2}{200 \text{ mA}} = \frac{\pi/10}{\pi/3} = \frac{3}{10}$$

$$\Rightarrow i_2 = 60 \text{ mA}$$

**5. Ans. (4)**
**Sol.** From KVL,

$$V_1 + V_2 - V_3 = 0 \Rightarrow V_1 + V_2 = V_3$$

**6. Ans. (2)**
**Sol.** Given that

$$\text{Current } I = I_0 + \beta t$$

$$I_0 = 20 \text{ A}; \beta = 3 \text{ A/s}$$

$$I = 20 + 3t; \frac{dq}{dt} = 20 + 3t$$


$$\int_0^q dq = \int_0^{20} (20 + 3t) dt; q = \int_0^{20} 20 dt + \int_0^{20} 3t dt$$

$$q = \left[ 20t + \frac{3t^2}{2} \right]_0^{20} = 1000 \text{ C}$$

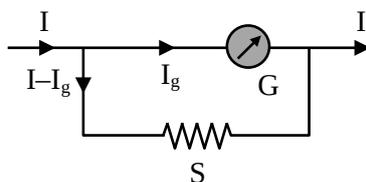**7. Ans. (3)**
**Sol.** Given  $G = 10 \Omega$ 

$$I_g = 3 \text{ mA}; I = 8 \text{ A}$$

In case of conversion of galvanometer into ammeter.




$$\text{We have } I_g G = (I - I_g) S$$

$$S = \frac{I_g G}{I - I_g}; S = \frac{(3 \cdot 10^{-3}) 10}{8 - 0.003}$$


$$= 3.75 \times 10^{-3} \Omega$$

**8. Ans. (2)**
**Sol.** Let  $x = \text{current/division}$ 

$$I_g = 25x$$

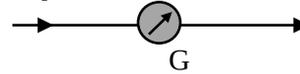


After applying shunt

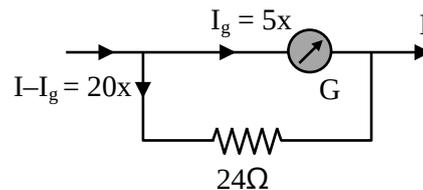

$$\text{Now } 5x \times G = 20x \times 24$$

$$G = 4 \times 24$$

$$G = 96 \Omega$$

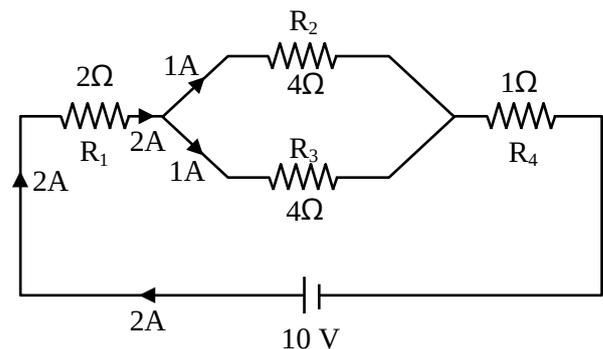
**9. Ans. (1)**
**Sol.**


$$R_{eq} = 2 \Omega + 2 \Omega + 1 \Omega = 5 \Omega$$

$$i = \frac{V}{R_{eq}} = \frac{10}{5} = 2 \text{ A}$$

$$\text{Current in resistance } R_3 = 2 \cdot \left( \frac{4}{4+4} \right)$$

$$= 2 \cdot \frac{4}{8} = 1 \text{ A}$$

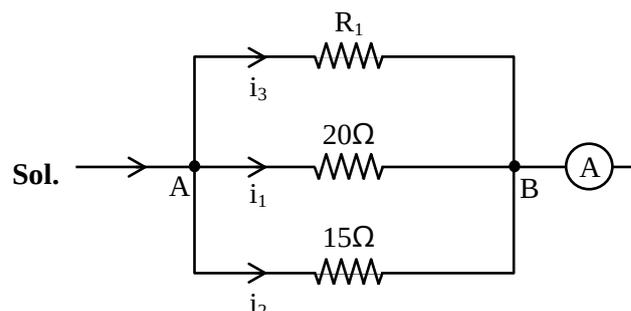**10. Ans. (30)**


**CURRENT ELECTRICITY**

Given,  $i_1 = 0.3 \text{ A}$ ,  $i_1 + i_2 + i_3 = 0.9 \text{ A}$   
 So,  $V_{AB} = i_1 \times 20\Omega = 20 \times 0.3 \text{ V} = 6 \text{ V}$   
 $i_2 = \frac{6\text{V}}{15\Omega} = \frac{2}{5} \text{ A}$ ;  $i_1 + i_2 + i_3 = \frac{9}{10} \text{ A}$   
 $\frac{3}{10} + \frac{2}{5} + i_3 = \frac{9}{10}$ ;  $\frac{7}{10} + i_3 = \frac{9}{10}$   
 $i_3 = 0.2 \text{ A}$   
 So,  $i_3 \times R_1 = 6 \text{ V}$   
 $(0.2)R_1 = 6$   
 $R_1 = \frac{6}{0.2} = 30 \Omega$

**11. Ans. (3)**

**Sol.**  $R_{eq} = 4000 \Omega$

$$i = \frac{4}{4000} = \frac{1}{1000} \text{ A}$$

$$V_0 = i.R = \frac{1}{1000} \cdot 500 = 0.5\text{V}$$

**12. Ans. (3)**


**Sol.**  $R_{T=27} = 60\Omega$ ,  $R_T = \frac{220}{2.75} = 80\Omega$

$$R = R_0 (1 + \alpha\Delta T)$$

$$80 = 60 [1 + 2 \times 10^{-4}(T-27)]$$

$$T \approx 1694^\circ\text{C}$$

**13. Ans. (6)**

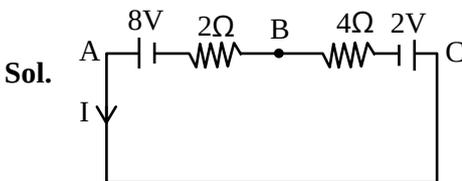

$$I = \frac{8-2}{2+4} = \frac{6}{6} = 1\text{A}$$

Applying Kirchoff from C to B

$$V_C - 2 - 4 \cdot 1 = V_B$$

$$V_C - V_B = 6\text{V} = 6\text{V}$$

**14. Ans. (4)**


**Sol.**  $\frac{v^2}{R} = W \dots(i)$

$$\frac{v^2}{\frac{1}{2}\left(\frac{R}{2}\right)} = W' \dots(ii)$$

From (i) & (ii), we get

$$W' = 4W$$

**15. Ans. (200)**

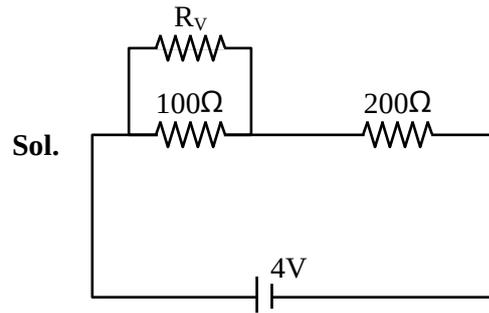

$$\frac{R_v \cdot 100}{R_v + 100} = \frac{200}{3}$$

$$3R_v = 2R_v + 200$$

$$R_v = 200$$

**16. Ans. (2)**

**Sol. Series :**

$$R_{eq} = R_1 + R_2$$

$$2R(1 + \alpha_{eq}\Delta\theta) = R(1 + \alpha_1\Delta\theta) + R(1 + \alpha_2\Delta\theta)$$

$$2R(1 + \alpha_{eq}\Delta\theta) = 2R + (\alpha_1 + \alpha_2)R\Delta\theta$$

$$\alpha_{eq} = \frac{\alpha_1 + \alpha_2}{2}$$

**Parallel :**

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{\frac{R}{2}(1 + \alpha_{eq}\Delta\theta)} = \frac{1}{R(1 + \alpha_1\Delta\theta)} + \frac{1}{R(1 + \alpha_2\Delta\theta)}$$

$$\frac{2}{1 + \alpha_{eq}\Delta\theta} = \frac{1}{1 + \alpha_1\Delta\theta} + \frac{1}{1 + \alpha_2\Delta\theta}$$

$$\frac{2}{1 + \alpha_{eq}\Delta\theta} = \frac{1 + \alpha_2\Delta\theta + 1 + \alpha_1\Delta\theta}{(1 + \alpha_1\Delta\theta)(1 + \alpha_2\Delta\theta)}$$

$$2[(1 + \alpha_1\Delta\theta)(1 + \alpha_2\Delta\theta)]$$

$$= [2 + (\alpha_1 + \alpha_2)\Delta\theta] [1 + \alpha_{eq}\Delta\theta]$$

$$2[1 + \alpha_1\Delta\theta + \alpha_2\Delta\theta + \alpha_1\alpha_2\Delta\theta^2]$$


$$= 2 + 2(\alpha_1 + \alpha_2)\Delta\theta + \alpha_{eq}(\alpha_1 + \alpha_2)\Delta\theta^2$$

Neglecting small terms



$$2 + 2(\alpha_1 + \alpha_2)\Delta\theta = 2 + 2(\alpha_1 + \alpha_2)\Delta\theta + \alpha_{eq}(\alpha_1 + \alpha_2)\Delta\theta^2$$

$$\alpha_{eq} = \frac{\alpha_1 + \alpha_2}{2}$$

17. Ans. (1)

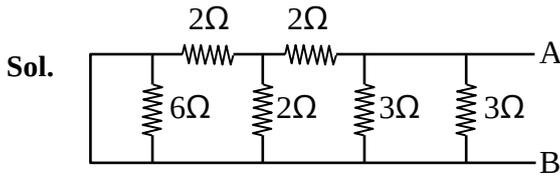


6Ω is short circuit

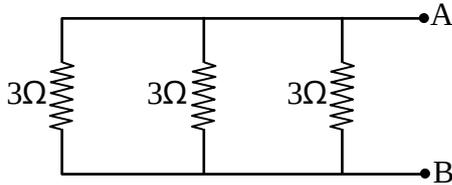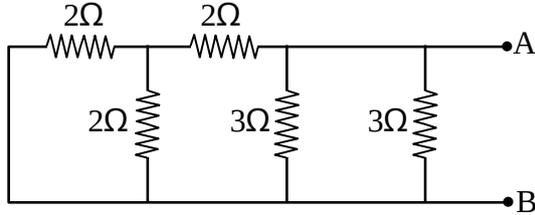

$$R_{eq} = 3 \cdot \frac{1}{3} = \Omega$$

18. Ans. (4)

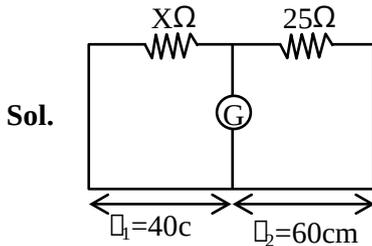

$$\frac{25}{r l_1} = \frac{X}{r l_2} \quad \dots (i)$$

$$\frac{25}{2r l_1'} = \frac{X}{2r l_2'} \quad \dots (ii)$$

From (i) and (ii)

$$l_2' = l_2 = 40 \text{ cm}$$

19. Ans. (3)

Sol.  $P = i^2 R$

$$P_{int} = I_{int}^2 R$$

$$P_{final} = (0.8 I_{int})^2 R$$

% change in power =

$$\frac{P_{final} - P_{int}}{P_{int}} \cdot 100 = (0.64 - 1) \cdot 100 = -36\%$$

20. Ans. (3)

Sol.  $R_{eq} = \frac{4}{3} \Omega$

$$\therefore P = \frac{V^2}{R_{eq}} = \frac{4}{4/3} = 3 \text{ W}$$

21. Ans. (3)


Sol.  $i = \frac{E_{eq}}{r_{eq}} = \frac{8 \cdot 5}{8 \cdot 0.2}$

$$I = 25 \text{ A}$$

$$V = E - ir$$

$$= 5 - 0.2 \times 25 = 0$$

22. Ans. (3)

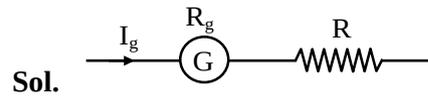

$$R = \frac{V}{I_g} - R_g = \frac{100}{5 \cdot 10^{-3}} - 50$$

$$= 20000 - 50$$

$$= 19950 \Omega$$


23. Ans. (22)

Sol.  $q = \int_1^2 i dt = \int_1^2 (3t^2 + 4t^3) dt$

$$q = (t^3 + t^4) \Big|_1^2; q = 22 \text{ C}$$

24. Ans. NTA (1)

Allen (Bonus)

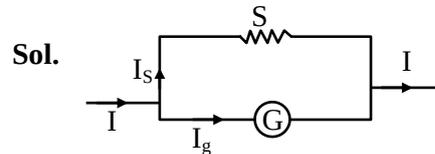

$$I_S S = I_g G$$

$$\frac{95}{100} I S = \frac{5I}{100} G; S = \frac{G}{19}$$

$$R_A = \frac{SG}{S+G} = \frac{\frac{G^2}{19}}{\frac{20G}{19}}$$

$$R_A = \frac{G}{20}$$

25. Ans. (3)

Sol. For no deflection  $\frac{0.8}{1} = \frac{R}{3}$

$$\Rightarrow R = 2.4 \text{ m}\Omega$$


Temperature fall in 10s = 20°C

$$R = R \alpha t$$

$$\alpha = \frac{\Delta R}{R \Delta t} = \frac{-0.6}{3 \cdot 20} = -10^{-2} \text{ C}^{-1}$$

**CURRENT ELECTRICITY**

26. **Ans. (1)**

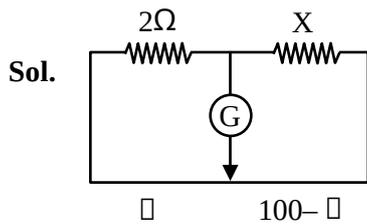

First case  $\frac{2}{40} = \frac{X}{60} \Rightarrow X = 3\Omega$

In second case  $X' = \frac{2 \cdot 3}{2+3} = 1.2\Omega$

$$\frac{2}{100 - X} = \frac{1.2}{100 - X}$$

$$200 - 2X = 1.2X$$

$$X = \frac{200}{3.2} = 62.5\text{cm}$$

Balance length changes by 22.5 cm

27. **Ans. (2)**

**Sol.** Given  $R_0 = 8\Omega, R_{100} = 10\Omega$

$$\therefore R_{100} = R_0 (1 + \alpha\Delta T)$$

$$\text{Also, } R_{400} = R_0 (1 + \alpha\Delta T^1)$$

$$\therefore 10 = 8 (1 + \alpha \times 100) \Rightarrow 100\alpha = \frac{1}{4}$$

$$\therefore R_{400} = 8 (1 + 400\alpha) = 8 (1 + 1) = 16\Omega$$

Hence option (2)

28. **Ans. (4)**

**Sol.** Let potential gradient be  $\lambda$ .

$$\therefore i \times 10 = \lambda \times 500 = \epsilon - ir_s$$

$$\Rightarrow 500\lambda = \epsilon - 50\lambda r_s$$

Also,


$$i' \times 1 = \lambda \times 400 = \epsilon - i'r_s$$

$$\Rightarrow 400\lambda = \epsilon - 400\lambda r_s$$

$$\therefore 100\lambda = 350\lambda r_s \Rightarrow r_s = \frac{10}{35} \approx 0.3\Omega$$

Hence option (4)

29. **Ans. (1)**

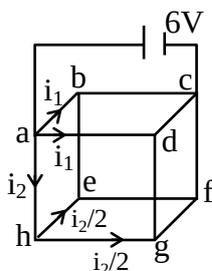

**Sol.**

From symmetry, current through e-b & g-d = 0

$$\therefore R_{eq} = \frac{3}{4} \cdot R = \frac{3}{2}\Omega$$

$$\therefore \text{Current through battery} = \frac{6 \cdot 2}{3} = 4A$$

$$i_2 = \frac{4}{8} \cdot 2 = 1A$$

$$\therefore \Delta V \text{ across e-f} = \frac{i_2}{2} \cdot R = \frac{1}{2} \cdot 2 = 1V$$

30. **Ans. (1)**

**Sol.** Rated power & voltage gives resistance

$$R = \frac{V^2}{P} = \frac{(200)^2}{50} = \frac{40000}{50}$$

$$R = 800$$

$$P = \frac{(V_{\text{applied}})^2}{R} = \frac{(100)^2}{800}$$

$$P = 12.5 \text{ watt}$$

Hence option 1 is correct.

31. **Ans. (32)**

$$\text{Sol. } \therefore R = \frac{\rho L}{A} = \frac{\rho V}{A^2} \therefore \frac{R_A}{R_B} = \frac{A_B^2}{A_A^2} = \frac{r_B^4}{r_A^4}$$

$$\Rightarrow \frac{R_A}{2} = \left[ \frac{4 \cdot 10^{-3}}{2 \cdot 10^{-3}} \right]^4$$

$$\Rightarrow R_A = 32 \Omega.$$

32. **Ans. (4)**

**Sol.** Here  $R_2, R_3, R_4$  are in parallel

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$R_{234} = 2\Omega$$

$R_{234}$  is in series with  $R_1$  so

$$R_{eq} = R_{234} + R_1 = 2 + 10 = 12\Omega$$

$$i = \frac{12}{12} = 1\text{Amp}$$

33. **Ans. (5)**

**Sol.**  $i = K\theta$

$$\frac{2}{GR} = K\theta$$

$$\Rightarrow \frac{1}{\theta} \cdot \frac{(GR)K}{2} = R \left( \frac{K}{2} \right) + \frac{KG}{2}$$

$$\text{Slope} = \frac{K}{2} = \frac{1}{4} \Rightarrow K = 0.5 = 5 \cdot 10^{-1} A$$

34. **Ans. (3)**

$$\text{Sol. } i_g = \frac{10}{400+100} = 20 \cdot 10^{-3} A$$

For ammeter

Let shunt resistance = S


$$i_g R = (i - i_g) S$$

$$20 \times 10^{-3} \times 100 = 10 S$$

$$S = 20 \times 10^{-2} \Omega$$

35. **Ans. (2)**

**Sol.**

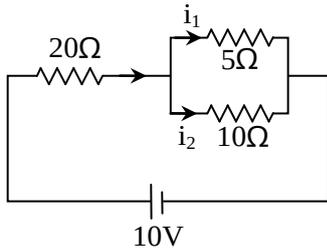


$$\frac{i_1}{i_2} = \frac{10}{5} = \frac{2}{1}$$

$$\frac{P_1}{P_2} = \frac{i_1^2 R_1}{i_2^2 R_2} = \left(\frac{2}{1}\right)^2 \cdot \frac{5}{10} = \frac{2}{1}$$

36. **Ans. (5)**

**Sol.**

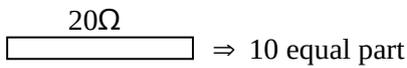

Each part has resistance =  $2\Omega$


2 parts are connected in parallel so,  $R = 1\Omega$

Now, there will be 5 parts each of resistance  $1\Omega$ , they are connected in series.

$$R_{eq} = 5R, R_{eq} = 5\Omega$$

37. **Ans. (3)**

**Sol.**

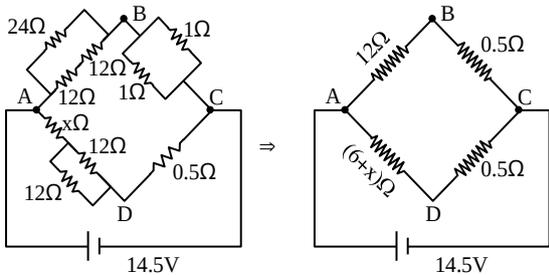

In case of balanced Wheatstone Bridge

$$\frac{V_{AB}}{V_{AD}} = \frac{V_{BC}}{V_{CD}} \Rightarrow \frac{12}{6+x} = \frac{0.5}{0.5}$$

$$x = 6\Omega$$

38. **Ans. (16)**

**Sol.** We know  $R = \frac{\rho l}{A}$ ,  $R \propto \frac{l}{r^2}$

As we stretch the wire, its length will increase but its radius will decrease keeping the volume constant

$$V_i = V_f$$

$$\pi r^2 l = \pi \frac{r^2}{4} l_f; l_f = 4l$$

$$\frac{R_{new}}{R_{old}} = \left(\frac{4l}{\frac{r^2}{4}}\right) \frac{r^2}{l} = 16$$

$$R_{new} = 16R \therefore x = 16$$

39. **Ans. (1)**

**Sol.** Power (P) = V.I

$$\Rightarrow 110 = (220)(I) \Rightarrow I = 0.5 \text{ A}$$


$$\text{Now, } I = \frac{n e}{t}$$

$$\Rightarrow 0.5 = \left(\frac{n}{t}\right) (1.6 \times 10^{-19})$$

$$\Rightarrow \frac{n}{t} = \frac{0.5}{1.6 \cdot 10^{-19}} \Rightarrow \boxed{\frac{n}{t} = 31.25 \cdot 10^{17}}$$

40. **Ans. (160)**

**Sol.**

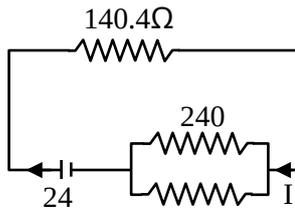

$$R_{eq} = 140.4 + \frac{240 \cdot 10}{240 + 10}$$

$$R_{eq} = 140.4 + \frac{2400}{250}$$


$$R_{eq} = 150\Omega$$

$\therefore$  Current in ammeter

$$= \frac{24}{150} = 160 \text{ mA}$$

41. **Ans. (1)**

**Sol.**

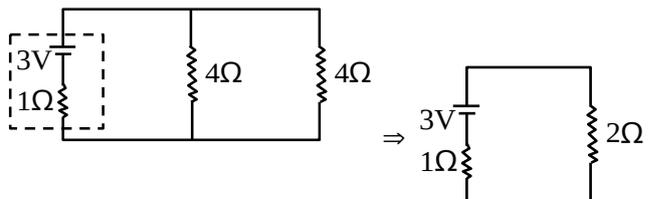

$$i = \frac{3}{1+2} = 1 \text{ A}$$

$$v = E - ir = 3 - 1 \times 1 = 2 \text{ V}$$

**CURRENT ELECTRICITY**
**42. Ans. (748)**
**Sol.**  $R = R_0(1 + \alpha\Delta T)$ 

$$\frac{\Delta R}{R_0} = \alpha\Delta T$$

**Case-I**
 $0^\circ\text{C} \rightarrow 100^\circ\text{C}$ 

$$\frac{10.2 - 10}{10} = \alpha(100 - 0) \quad \dots (1)$$

**Case-II**
 $0^\circ\text{C} \rightarrow t^\circ\text{C}$ 

$$\frac{10.95 - 10}{10} = \alpha(t - 0) \quad \dots (2)$$

$$\Rightarrow \frac{t}{100} = \frac{0.95}{0.2} = 475^\circ\text{C}$$


$$t = 475 + 273 = 748\text{ K}$$

**43. Ans. (5)**
**Sol.**  $R_{\text{heater}} = \frac{V^2}{P} = \frac{(100)^2}{1000} = 10\Omega$ 

$$\text{For heater } P = \frac{V^2}{R} \Rightarrow V = \sqrt{PR}$$

$$V = \sqrt{62.5 \cdot 10}$$

$$V = 25\text{ v}$$

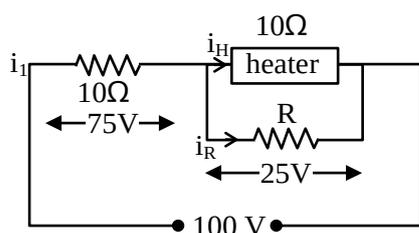

$$i_1 = \frac{75}{10} = 7.5\text{A}, \quad i_H = \frac{25}{10} = 2.5\text{ A.}$$

$$i_R = i_1 - i_H = 5$$

$$V = IR$$

$$R = \frac{25}{5} = 5\Omega$$



**44. Ans. (2)**
**Sol.**  $G = 200\Omega$ 

$$i_g = 20 \mu\text{A}$$


$$i = i_g \left( \frac{G}{S} + 1 \right)$$

$$\Rightarrow 20 \times 10^{-3} = 20 \times 10^{-6} \left( \frac{200}{S} + 1 \right)$$

$$\Rightarrow \frac{200}{S} = 999 \Rightarrow S \approx 0.2\Omega$$

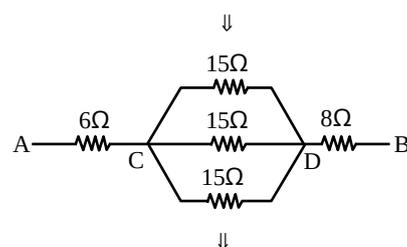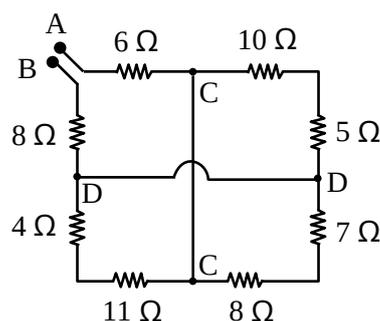**45. Ans. (4)**
**Sol.**


$$\Rightarrow R_{\text{eq}} = 6\Omega + 5\Omega + 8\Omega = 19\Omega$$

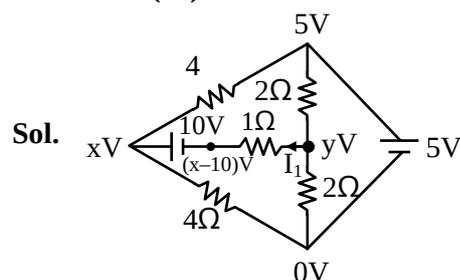**46. Ans. (25)**


$$\frac{y-5}{2} + \frac{y-0}{2} + \frac{y-x+10}{1} = 0$$

$$y-5+y+2y-2x+20=0$$

$$4y-2x+15=0 \quad \dots (i)$$

$$\frac{x-5}{4} + \frac{x-0}{4} + \frac{x-10-y}{1} = 0$$

$$x-5+x+4x-40-4y=0$$

$$6x-4y-45=0 \quad \dots (ii)$$

$$\frac{-2x+4y+15=0 \quad \dots (ii)}{4x-30=0}$$

$$x = \frac{15}{2} \quad \& \quad 4y - 15 + 15 = 0$$

$$y = 0$$

$$i = \frac{y-x+10}{1}$$

$$i = \frac{0-7.5+10}{1}$$

$$i = 2.5\text{A} = \frac{n}{10}\text{A}; \quad n = 25$$

47. Ans. (2500)

Sol.  $R_{eq} = \frac{10^4 R}{10^4 + R}$

$E = 4V, I = 2mA$

$I = \frac{E}{R_{eq}} \Rightarrow 2 \cdot 10^{-3} = \frac{4(10^4 + R)}{10^4 R}$

$\Rightarrow 20R = 40000 + 4R$



$16R = 40000$

$R = 2500\Omega$

48. Ans. (2)

Sol. From symmetry we can remove two middle resistance.

New circuit is

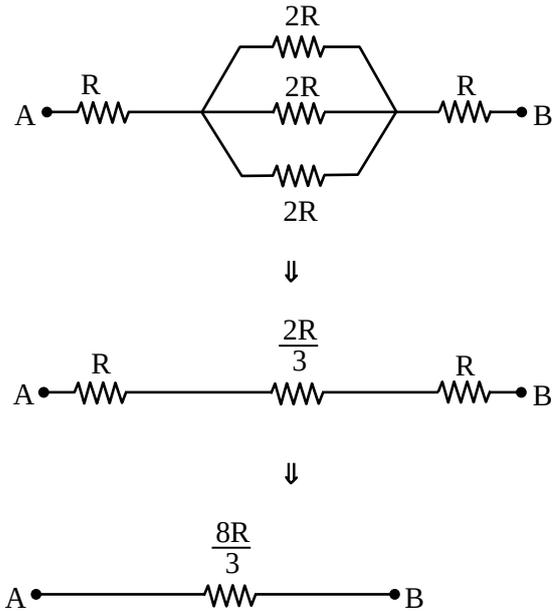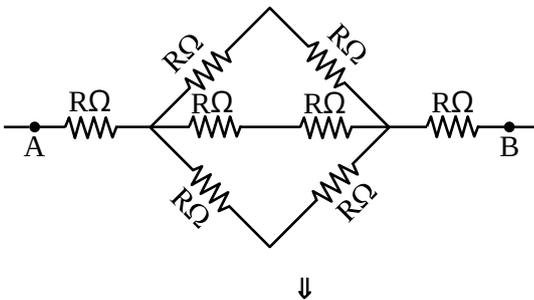

49. Ans. (1027)

Sol.  $R = R_0(1 + \alpha\Delta T)$

$62 = 50 [1 + 2.4 \times 10^{-4} T]$

$T = 1000^\circ C$

$\Rightarrow T - 27^\circ = 1000^\circ C$

$T = 1027^\circ C$